

# Counters

- ▶ A counter is a circuit whose outputs go through a prescribed sequence of values and repeats over and over. The outputs of the counter are held at the outputs of flip flops.
- ▶ The change from one value to the next value happens on the arrival of the active edge of some signal; e.g., a clock signal.
- ▶ Counters come in two varieties: *asynchronous* and *synchronous* counters.
- ▶ We will consider mainly synchronous counters.

# Asynchronous counters

- ▶ Asynchronous counters are characterized by the observation that different signals drive different clock inputs on different flip flops. This means that the outputs of each flip flop *do not change at the same time are not synchronized with some master clock.*

# Asynchronous binary ripple counter


- ▶ Design a 3-bit counter that counts  $0, 1, \dots, 7$  and repeats. The circuit should have a signal  $en$  such that  $en = 1$  the circuit should count upon the arrival of the active clock edge. When  $en = 0$ , the circuit should not count (hold its current value).
- ▶ Can figure this out by looking at the sequence of numbers we want to produce (ignore the  $en$  input for the moment and assume the counter is always counting...)

current count			next count			
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$	
0	0	0	0	0	1	
0	0	1	0	1	0	
0	1	0	0	1	1	
0	1	1	1	0	0	
1	0	0	1	0	1	
1	0	1	1	1	0	
1	1	0	1	1	1	
1	1	1	0	0	0	$\leftarrow$ repeat

- ▶ Observations: i)  $a_0$  always toggles; ii)  $a_1$  toggles when  $a_0 = 1 \rightarrow 0$ ; iii)  $a_2$  toggles when  $a_1 = 1 \rightarrow 0$ .
- ▶ In other words, the  $i$ -th bit toggles when the  $(i - 1)$ -th bit makes a transition from  $1 \rightarrow 0$ .
 
# Asynchronous binary ripple counter

- ▶ The observation that outputs need to toggle motivates the use of *TFFs*. The observation that things toggle when a signal changes  $1 \rightarrow 0$  motivates using these signals as inputs to flip flop clock inputs.
- ▶ The circuit...



- ▶ Note the creative use of the enable signal... If  $en = 0$  all inputs to the toggle flip flops is 0 and the flip flops will not toggle.

# Asynchronous binary ripple counter

- ▶ If we don't care about how fast the circuit works, then there is really no problem with this sort of counter.
- ▶ However, it can be *slow* if the number of bits is very large. Here's why...
  - ▶ Consider the number of bits  $n$  to be very large (e.g., 128 or something like that).
  - ▶ Further, consider all of the flip flops to be 1; the next count value is 0 and *all flip flop outputs need to toggle*.
  - ▶ See the problem?
  - ▶ Output  $a_0$  must toggle (and it takes  $T_{co}$  for  $a_0$  to change...), then  $a_1$  will toggle (and it takes another  $T_{co}$  for  $a_1$  to change), then  $a_2$  will toggle (and it takes another  $T_{co}$  for  $a_2$  to change), and so on...
- ▶ Because every flip flop is clocked by a different clock and the clocks form a *chain*, this counter can be quite slow.
- ▶ Better to create a circuit in which all flip flop outputs change at the same time.

# Synchronous counters

- ▶ Synchronous counters are characterized by the observation that a single clock signal is used to clock every flip flop. This means that all the flip flop outputs *change simultaneously and are synchronized with the clock*.

# Synchronous binary up counter


- ▶ Design a 3-bit synchronous binary up counter with an enable input  $en$ . When  $en = 0$ , the counter should not count. When  $en = 1$ , the circuit should count upon the arrival of the active clock edge. The output sequence always increases by 1 and repeats over and over...
- ▶ Design using intuition... Consider the count sequence for a binary up counter and assume that  $en = 1$ ...

current count			next count			
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$	
0	0	0	0	0	1	
0	0	1	0	1	0	
0	1	0	0	1	1	
0	1	1	1	0	0	
1	0	0	1	0	1	
1	0	1	1	1	0	
1	1	0	1	1	1	
1	1	1	0	0	0	← repeat

- ▶ Observations: i)  $a_0$  always toggles; ii)  $a_1$  toggles when the current value of  $a_0 = 1$ ; iii)  $a_2$  toggles when the current value of  $a_1a_0 = 11$ .
- ▶ In other words,  $a_i$  should toggle when bits  $a_{i-1}$  down to  $a_0$  are all 1. This would apply for a binary up counter with any number of bits.
 
# Synchronous binary up counter

- ▶ The observation that bits need to toggle motivates the use of *TFF*.
- ▶ Our circuit...



- ▶ Note the creative use of the enable signal... If  $en = 0$  all inputs to the *TFF* will be forced to 0 and they will not toggle. Otherwise, the inputs to the *TFF* are the conditions required for the flip flops to toggle appropriately.
- ▶ We could use set/reset control signals to initialize the counter to any *initial* state.



# Synchronous binary down counter


- ▶ Design a 3-bit synchronous binary down counter with an enable input  $en$ . When  $en = 0$ , the counter should not count. When  $en = 1$ , the circuit should count upon the arrival of the active clock edge. The count should always decrease by 1 and repeats over and over...
- ▶ Design using intuition... Consider the count sequence for a binary down counter and assume that  $en = 1$ ...

current count			next count			
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$	
1	1	1	1	1	0	
1	1	0	1	0	1	
1	0	1	1	0	0	
1	0	0	0	1	1	
0	1	1	0	1	0	
0	1	0	0	0	1	
0	0	1	0	0	0	
0	0	0	1	1	1	← repeat

- ▶ Observations: i)  $a_0$  always toggles; ii)  $a_1$  toggles when the current value of  $a_0 = 0$ ; iii)  $a_2$  toggles when the current value of  $a_1a_0 = 00$ .
- ▶ In other words,  $a_i$  should toggle when bits  $a_{i-1}$  down to  $a_0$  are all 0. This would apply for a binary down counter with any number of bits.
 
# Synchronous binary down counter

- ▶ The observation that bits need to toggle motivates the use of *TFF*.
- ▶ Our circuit...



- ▶ Note the creative use of the enable signal... If  $en = 0$  all inputs to the *TFF* will be forced to 0 and they will not toggle. Otherwise, the inputs to the *TFF* are the conditions required for the flip flops to toggle appropriately.
- ▶ We could use set/reset control signals to initialize the counter to any *initial* state.

# Synchronous binary up/down counter


- ▶ Can combine different operations together... Design a single circuit capable of counting either up or down according to the following:

Inputs		Action
<i>up</i>	<i>down</i>	
0	0	<i>don't count</i>
0	1	<i>count down</i>
1	X	<i>count up</i>

- ▶ The approach we can take... Use circuits we already know and then add extra circuitry to control what signal gets to the inputs of the flip flops *depending on the operation we want to perform*.
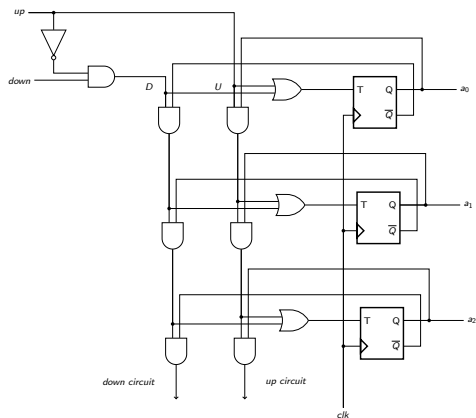
# Synchronous binary up/down counter

- Our circuit... includes both the binary up counter circuitry, the binary down counter circuitry and extra logic to control the operation...



- The extra gates and control logic are effectively performing a multiplexer operation to get the correct signal to the input of the flip flop.
- Consider the signals  $D$  and  $U$  in the circuit — these are the enable signals for the down counter and up counter, respectively... Think about it...

# Synchronous binary up/down counter with parallel load


- ▶ Design a binary up/down counter that also has the ability to load an arbitrary value.
- ▶ This requires another control line and results in a new table of operation:

Inputs			Action
<i>load</i>	<i>up</i>	<i>down</i>	
0	0	0	<i>hold</i>
0	0	1	<i>count down</i>
0	1	X	<i>count up</i>
1	X	X	<i>load</i>

- ▶ The approach we can take... Use circuits we already know and then add extra circuitry to control what signal gets to the inputs of the flip flops *depending on the operation we want to perform*.

# Synchronous binary up/down counter with parallel load


- The circuit...

 

- The extra gates and control logic are effectively performing a multiplexer operation to get the correct signal to the input of the flip flop.
- **Q:** What is the purpose of the **XOR** gates? **A:** Since we are using *TFF*, we need to *compare*  $i_j$  and  $a_j$  to decide how to load (do we need to invert  $a_j$  or not?).
 
# Counter symbols

- We might have a symbol for a counter... Likely accompanied by a table explaining its operation.



<i>clr</i>	<i>ld</i>	<i>cnt</i>	<i>clk</i>	Function
0	X	X	X	Output to zero
1	1	X	↑	Parallel load
1	0	1	↑	Count up
1	0	0	↑	Hold


# Modulo counter

- ▶ If we don't want to count through the entire binary sequence, then we might want to build a *modulo counter*. A modulo- $n$  counter would count  $0, 1, \dots, n - 1$  and repeat.
- ▶ We could also decide to start the count sequence at some value other than 0.
- ▶ Could design such a counter from scratch or use a “off-the-shelf” binary counter and make modifications.
  - ▶ Take a binary counter and add additional logic to detect when we have reached our maximum count.
  - ▶ Then, upon the next clock cycle, do a parallel load to restart the count sequence.


 
# Modulo counter

- ▶ Example... design a counter that counts 2, 3,  $\dots$ , 9 and then repeats.
- ▶ Solution...




- ▶ When this circuit hits 9, the output of the **AND** gate will be 1 and the  $ld$  signal will be active. At the next active clock edge, the circuit will load the binary value of 2 and start counting correctly.
- ▶ Also added a  $start$  signal to be able to reset the counter and start counting from 2.

# Generic counter design


- ▶ Counter design can also be generic — we can design a counter which counts in any sequence we want. Further, we can use any type of flip flop.
- ▶ To do this, we can start by drawing a version of a *state diagram* to illustrate the count sequence.
- ▶ Example... design a counter which counts in the sequence  $3 \rightarrow 6 \rightarrow 0 \rightarrow 1 \rightarrow 7$  and repeats.

# Generic counter design

- ▶ The state diagram...

 

 - ▶ The state diagram in terms of binary values...



- ▶ Each bubble represents a state. Each edge tells us how we transition from state to state when the active clock edge arrives.
- ▶ The values (at least in the second state diagram) is the required circuit output — it tells us that we need 3 flip flops for this counter (one flip flop for each bit).

# Generic counter design

- ▶ We can convert this diagram to a table which is a version of a *state table*. The state table shows the *current state* and the *next state*. More or less, the *current state* represents the current output of the flip flops (so the current count value) and the *next state* is what the flip flop outputs need to change to (so the next count value).
- ▶ The *state table*...

Current State			Next State		
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$
0	1	1	1	1	0
1	1	0	0	0	0
0	0	0	0	0	1
0	0	1	1	1	1
1	1	1	0	1	1

- ▶ Again, this table tells us how the flip flop outputs need to change when the active clock edge arrives.

# Generic counter design

- Assume we want to use *DFF*... Recall how they work:

$D$	$Q(t+1)$
0	0
1	1

or

$D$	$Q(t) \rightarrow Q(t+1)$
0	$0 \rightarrow 0$
0	$1 \rightarrow 0$
1	$0 \rightarrow 1$
1	$1 \rightarrow 1$

- The table assuming we want to use *DFF*...

Current State			Next State			Inputs for <i>DFF</i>		
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$	$d_2$	$d_1$	$d_0$
0	1	1	1	1	0	1	1	0
1	1	0	0	0	0	0	0	0
0	0	0	0	0	1	0	0	1
0	0	1	1	1	1	1	1	1
1	1	1	0	1	1	0	1	1

# Generic counter design

- We can use the *DFF* inputs to write down equations for each of the *DFF* inputs... We could use Karnaugh maps to get these equations...


$$d_2 = a_2' a_0$$

$$d_1 = a_0$$

$$d_0 = a_1' + a_2 a_0$$

# Generic counter design

- The counter using *DFF*...

 

- What is not shown is that we should use the set and reset inputs on the *DFFs* in order to ensure that we can start the count sequence at 3.

# Generic counter design

- Assume we want to use *TFF*... Recall how they work:

$T$	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

or

$T$	$Q(t) \rightarrow Q(t+1)$
0	$0 \rightarrow 0$
0	$1 \rightarrow 1$
1	$0 \rightarrow 1$
1	$1 \rightarrow 0$

- The table assuming we want to use *TFF*...

Current State			Next State			Inputs for <i>TFF</i>		
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$	$t_2$	$t_1$	$t_0$
0	1	1	1	1	0	1	0	1
1	1	0	0	0	0	1	1	0
0	0	0	0	0	1	0	0	1
0	0	1	1	1	1	1	1	0
1	1	1	0	1	1	1	0	0



# Generic counter design

- We can use the *TFF* inputs to write down equations for each of the *TFF* inputs... We could use Karnaugh maps to get these equations...


$$t_2 = a_2 + a_0$$

$$t_1 = a_1 \oplus a_0$$

$$t_0 = a_2' a_0' + a_2' a_1 = a_2' (a_0' + a_1)$$

# Generic counter design

- The counter using *TFF*...

 

- What is not shown is that we should use the set and reset inputs on the *TFFs* in order to ensure that we can start the count sequence at 3.

# Generic counter design

- Assume we want to use *JKFF*... Recall how they work: Recall how a JK flip flop works.

$J$	$K$	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

or

$J$	$K$	$Q(t) \rightarrow Q(t+1)$
0	X	$0 \rightarrow 0$
X	0	$1 \rightarrow 1$
1	X	$0 \rightarrow 1$
X	1	$1 \rightarrow 0$

- The table assuming we want to use *JKFF*...

Current State			Next State			Inputs for <i>JKFF</i>		
$a_2$	$a_1$	$a_0$	$a_2$	$a_1$	$a_0$	$j_2 k_2$	$j_1 k_1$	$j_0 k_0$
0	1	1	1	1	0	1X	X0	X1
1	1	0	0	0	0	X1	X1	0X
0	0	0	0	0	1	0X	0X	1X
0	0	1	1	1	1	1X	1X	X0
1	1	1	0	1	1	X1	X0	X0


# Generic counter design

- ▶ We can use the *JKFF* inputs to write down equations for each of the *JKFF* inputs... We could use Karnaugh maps to get these equations...

$$\begin{aligned}j_2 &= a_0 \\k_2 &= 1 \\j_1 &= a_0 \\k_1 &= a_0' \\j_0 &= a_2 \\k_0 &= a_2 a_1\end{aligned}$$

## Generic counter design

- ▶ The counter using *JKFF*...

 

- ▶ What is not shown is that we should use the set and reset inputs on the JKFFs in order to ensure that we can start the count sequence at 3.

# Generic counter design

- ▶ The type of flip flop we select has an impact on the *complexity* of the circuit we end up with (that is, how much logic gates we need to produce the inputs to the flip flops).
- ▶ In this example, using *DFF* wasn't any more or less complex than using *TFF*. This might not always be the case!
- ▶ However, using *JKFF* resulted in almost no extra logic gates. *JKFF* are a bit more difficult to work with, but often result in less combinational logic — it's because *JKFF* has a lot of don't care situations when considering the required inputs to cause the outputs to change as required.