

# ECE 124 digital circuits and systems

## Assignment #5

Q1: In class we designed a comparator for two,  $n$ -bit unsigned binary numbers  $A$  and  $B$  by deriving 2 level SOP for  $(A = B)$ ,  $(A > B)$  and  $(A < B)$ . Such circuits can require logic gates with many inputs as  $n$  increases.

Another way to make a comparator is to design a block which can be replicated  $n$  times; this is shown below. Determine the logic inside of each block which will compare two,  $n$ -bit unsigned binary numbers.

 


Figure 1: An  $n$ -bit comparator made from  $n$  identical sub-circuits.

- Q2: Given the solution to Question 1, how long (in terms of gate delays) does it take to compare two,  $n$ -bit numbers?
- Q3: Given the solution to Question 1 and 2, how would you design a comparator circuit that is faster than the comparator designed in Question 1, but uses logic gates with a reasonable number of inputs?
- Q4: Implement the following 3-input binary functions using 3-to-8 decoders and an OR gate.

(a)  $f(a, b, c) = \sum(0, 2, 3, 4, 5, 7).$

(b)  $f(a, b, c) = \sum(1, 2, 3, 5, 6).$

Q5: Implement the following logic functions using a 2-to-1 multiplexer and as few additional logic gates as possible.

(a)  $f = a'c' + bc' + a'b.$

(b)  $f = b'c' + ab.$

Q6: Implement the 4-input logic function  $f(a, b, c, d) = \sum(0, 1, 3, 4, 8, 9, 15)$  using an 8-to-1 multiplexer.

Q7: Use Shannon expansion to derive an implementation for each of the following functions using a 2-to-1 multiplexer and any other necessary logic gates.

(a)  $f(a, b, c) = \sum(0, 2, 3, 6).$

(b)  $f(a, b, c) = \sum(0, 4, 6, 7).$

Q8: Use Shannon expansion to derive the minterms for each of the following expressions.

(a)  $f = b' + a'c' + ac.$

(b)  $f = b + a'c'.$

Q9: Shown in Figure 2 is a prefabricated block of logic. Show how the function  $f = bc' + ac + b'c$  can be implemented in this prefabricated block. You may also use the constants 0 and 1 if needed.

 


Figure 2: Prefabricated circuit block for Question 9.

Q10: Derive a circuit for an 8-to-3 priority encoder.

Q11: Implement a full adder using two 4-to-1 multiplexers.