

# ECE 124 digital circuits and systems

## Assignment #3

Q1: Find minimum SOP and POS expressions for the following functions using 3-variable Kmaps.

(a)  $f(a, b, c) = \sum(0, 2, 6, 7)$

(b)  $f(a, b, c) = \Pi(1, 2, 4)$

Q2: Find minimum SOP and POS expressions for the following functions using 3-variable Kmaps.

(a)  $f = xy + x'y'z' + x'yz'$

(b)  $f = A'B + BC' + B'C'$

(c)  $f = (x' + y + z)(x' + y + z')(x' + y' + z)$

Q3: Find minimum SOP and POS expressions for the following functions using 4-variable Kmaps.

(a)  $f = w'z + xz + x'y + wx'z.$

(b)  $f = B'D + A'BC' + AB'C + ABC'$

(c)  $f = (A' + B' + D')(A + B' + C')(A' + B + D')(B + C' + D').$

Q4: Find minimum SOP and POS expressions for the following functions using 4-variable Kmaps.

(a)  $f(w, x, y, z) = \sum(0, 1, 2, 3, 4, 12, 13, 14, 15)$

(b)  $f(w, x, y, z) = \Pi(0, 1, 2, 4, 5, 7, 8, 9, 10, 12, 14, 15)$

Q5: Find minimum SOP and POS expressions for the following functions using 5-variable Kmaps.

(a)  $f(x_1, x_2, x_3, x_4, x_5) = \sum(0, 1, 4, 5, 16, 17, 21, 25, 29)$

(b)  $f = x'_1x'_2x_3x'_4 + x'_1x'_2x'_3x'_4 + x'_2x'_4x'_5 + x'_2x_3x'_4 + x_3x_4x'_5 + x_2x_4x'_5.$

(c)  $f(x_1, x_2, x_3, x_4, x_5) = \Pi(1, 4, 6, 7, 9, 12, 15, 17, 20, 21, 22, 23, 28, 31)$

Q6: Find minimum SOP and POS expressions for the following functions together with the don't care conditions  $D$ .

(a)  $f(w, x, y, z) = \sum(0, 2, 8, 9, 10, 15) + D(1, 3, 6, 7)$

(b)  $f(w, x, y, z) = \Pi(1, 3, 5, 7, 13) + D(0, 2, 15)$

Q7: Find the prime implicants for the following functions. Determine which prime implicants are essential.

(a)  $f(a, b, c, d) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

(b)  $f(a, b, c, d) = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$

Q8: A four-variable logic function that equals 1 if any three or all four input variables are equal to 1 is called a *majority* function. Design a minimum cost SOP circuit that implements the majority function.

Q9: Derive a minimum cost 2-level circuit for a four variable function that is equal to 1 if exactly two or exactly three of its input variables are equal to 1; otherwise it is equal to 0.

Q10: A circuit with two outputs is required to implement the two logic functions  $f$  and  $g$  given by

$$f(a, b, c, d) = \sum(0, 2, 4, 6, 7, 9) + D(10, 11)$$

and

$$g(a, b, c, d) = \sum(2, 4, 9, 10, 15) + D(0, 13, 14)$$

where  $D$  denotes the don't cares for each function.

(a) Design a minimum SOP for both  $f$  and  $g$  separately and compute cost of each function assuming each gate costs 1 and each gate input costs 1. You may assume circuit inputs are available in both complemented and uncomplemented forms.

(b) Design a minimum cost circuit that implements both  $f$  and  $g$  as SOPs. Determine the cost of the circuit.

Q11: Repeat problem 10 for the following functions.

$$f(x_1, x_2, x_3, x_4, x_5) = \sum(1, 4, 5, 11, 27, 28) + D(10, 12, 14, 15, 20, 31)$$

and

$$g(x_1, x_2, x_3, x_4, x_5) = \sum(0, 1, 2, 4, 5, 8, 14, 15, 16, 18, 20, 24, 26, 28, 31) + D(10, 11, 12, 27)$$

Q12: Derive a minimum cost circuit that implements the function  $f(a, b, c, d) = \sum(4, 7, 8, 11) + D(12, 15)$ . You are not restricted to 2-level circuits and may use any sort of logic gate.

Q13: Find a minimum cost circuit that implements the function  $f(a, b, c, d) = \sum(0, 4, 8, 13, 14, 15)$ . The input variables are available in uncomplemented form only.

Q14: Find the simplest realization of the function  $f(a, b, c, d) = \sum(0, 3, 4, 7, 9, 10, 13, 14)$  assuming you can only use logic gates with a maximum of 2-inputs.