

ECE-124 Lab-3 Submission Form – Winter 2018

GROUP NUMBER: 15		Lab3 Demo	Lab3 Report	
SESSION NUMBER: 205		Out of 10	Out of 10	
NAME: (Print)	UW User ID (not Student ID)	Signature		
Partner A: Yeliang Shou	y2shou	yeliang		
Partner B: Yun Han Xiao	yhxiao	[Signature]		
LAB3 DESIGN DEMO		Marks Allotted	A	B
Desired Temp (sw[7..4]) is displayed on Digit1?		1	1	1
Current Temp (sw[3..0]) is displayed on Digit2?		1	1	1
Doors/Windows (PB[2..0]) displayed on LEDs[6..4]?		1	1	1
Furnace, Blower, System At Temp, A/C, Blower Indicators LEDs?		1	1	1
A/C ON & Blower ON when Current Temp > Desired Temp?		1	1	1
Furnace ON & Blower ON when Current Temp < Desired Temp?		1	1	1
A/C, Furnace, Blower turn OFF when Doors/Windows Open?		1	1	1
DISCUSSION: Comment on your VHDL Implementation?		3	3	3
LAB3 DESIGN REPORT (see rubric on LEARN for details)		Marks Allotted	TEAM	
All VHDL files (not the sevenseg_decoder or seg7_mux files). Structural VHDL design must be used at the Top Level.		2		
Comparator must have a <u>Boolean equation</u> per each output.				
Truth Table for 4-Bit Comparator Design with all entries inserted		2		
Part A Simulations of Comparator showing A>B, A=B, A<B		2		
RTL View of the Logic design (just of the Top Level)		2		
Total Design Logic Elements Used /8064		2		
Delay in Report Submission (-1 per day) x number of days:				
LAB3 REPORT MARK		Out of 10		

LogicalStep_Lab3.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity LogicalStep_Lab3_top is port (
    clk_in_50      : in  std_logic;
    pb             : in  std_logic_vector(3 downto 0);
    sw             : in  std_logic_vector(7 downto 0);
    leds          : out std_logic_vector(7 downto 0);
    seg7_data      : out std_logic_vector(6 downto 0);
    seg7_char1     : out std_logic;
    seg7_char2     : out std_logic
);
end LogicalStep_Lab3_top;

architecture Energy_Monitor of LogicalStep_Lab3_top is
    -- Components Used

    component Comp4 port(
        A      : in  std_logic_vector(3 downto 0);
        B      : in  std_logic_vector(3 downto 0);
        GT     : out std_logic;
        EQ     : out std_logic;
        LE     : out std_logic
    );
    end component;

    component SevenSegment port (
        hex      : in  std_logic_vector(3 downto 0);
        sevensseg : out std_logic_vector(6 downto 0)
    );
    end component;

    component segment7_mux port(
        clk      : in  std_logic := '0';
        DIN2     : in  std_logic_vector(6 downto 0);
        DIN1     : in  std_logic_vector(6 downto 0);
        DOUT     : out std_logic_vector(6 downto 0);
        DIG2     : out std_logic;
        DIG1     : out std_logic
    );
    end component;
```

In this first part, we declared the component including the 4 bits comparators (Comp4) and the muxes necessary for Character Display.

```

component Thermostat port(
    CT : in  std_logic_vector(3 downto 0);
    DT : in  std_logic_vector(3 downto 0);
    OP : in  std_logic_vector(2 downto 0);
    OTP : out std_logic_vector(6 downto 0)
);
end component;

-- Create any signals, or temporary variables to be used
signal thermo_otp : std_logic_vector(6 downto 0);
signal char1 : std_logic_vector(6 downto 0);
signal char2 : std_logic_vector(6 downto 0);

-- Here the circuit begins
begin

    --Thermostat instance will implement the logic
    --    it also incorporate the comparator inside
    |--    and output directly to the LEDs

    thermostatInstance : Thermostat port map( sw(3 downto 0),
                                                sw(7 downto 4),
                                                pb(2 downto 0),
                                                leds(6 downto 0));

    -- Displaying current and desired temperatures
    sevenmux1 : SevenSegment port map(sw(7 downto 4), char1);
    sevenmux2 : SevenSegment port map(sw(3 downto 0), char2);

    display : segment7_mux port map(
        clk_in_50,
        char1,
        char2,
        seg7_data,
        seg7_char1,
        seg7_char2
    );

end Enerav Monitor;

```

Here, we declared a Thermostat component which will be a sub-module responsible for handling the logic. We instantiate the Thermostat by mapping our input switches [7..4] as desired temperature and sw[3..0] as current temperature (each a 4 bit input). The output of the Thermostat will be directly mapped to the appropriate LED through the 7 bit LED vector. We have also instantiated the necessary components for the Seven Seg Display.

Compx4.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Compx4 is port(
    A      : in std_logic_vector(3 downto 0);
    B      : in std_logic_vector(3 downto 0);
    GT     : out std_logic;
    EQ     : out std_logic;
    LE     : out std_logic
);
end Compx4;

architecture logicCompx4 of Compx4 is

    component Compx1 port(
        ai : in std_logic;
        bi : in std_logic;

        go : out std_logic;
        eo : out std_logic;
        lo : out std_logic
    );
    end component;

    -- For each bit's output by index

    signal g3, g2, g1, g0 : std_logic;
    signal e3, e2, e1, e0 : std_logic;
    signal l3, l2, l1, l0 : std_logic;

begin

    inst0 : Compx1 port map(A(0), B(0), g0, e0, l0);
    inst1 : Compx1 port map(A(1), B(1), g1, e1, l1);
    inst2 : Compx1 port map(A(2), B(2), g2, e2, l2);
    inst3 : Compx1 port map(A(3), B(3), g3, e3, l3);

    EQ <= e0 and e1 and e2 and e3;
    GT <= g3 or
        (e3 and g2) or
        (e3 and e2 and g1) or
        (e3 and e2 and e1 and g0);
    LE <= l3 or
        (e3 and l2) or
        (e3 and e2 and l1) or
        (e3 and e2 and e1 and l0);

end architecture logicCompx4;
```

Here, we applied the 1-bit comparator to each of the 4 bits in input A and B, we then applied the necessary logical operation to obtain an overall result on Greater or Equal or Less.

Comp1.vhd

```

Library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Comp1 is port(
    ai      : in std_logic;
    bi      : in std_logic;

    go      : out std_logic;
    eo      : out std_logic;
    lo      : out std_logic
);
end Comp1;

architecture logicComp1 of Comp1 is
begin

    eo <= (ai and bi) or (not(ai) and not(bi));
    go <= ai and not(bi);
    lo <= not(ai) and bi;

end architecture logicComp1;

```

The one bit comparator is straightforward and trivial, if both bits are one or both are zero, then they are equal, if the A bit is one while the B is zero, we then have greater, conversely we will output “Less”.

Table 1: Logic Table for 4-bit Magnitude Comparator

A3 < B3	A3 = B3	A3 > B3	A2 < B2	A2 = B2	A2 > B2	A1 < B1	A1 = B1	A1 > B1	A0 < B0	A0 = B0	A0 > B0	A < B	A = B	A > B
0	0	1	X	X	X	X	X	X	X	X	X	0	0	1
1	0	0	X	X	X	X	X	X	X	X	X	1	0	0
0	1	0	0	0	1	X	X	X	X	X	X	0	0	1
0	1	0	1	0	0	X	X	X	X	X	X	1	0	0
0	1	0	0	1	0	0	0	1	X	X	X	0	0	1
0	1	0	0	1	0	1	0	0	0	X	X	1	0	0
0	1	0	0	1	0	0	1	0	0	0	1	0	0	1
0	1	0	0	1	0	0	0	1	0	1	0	1	0	0
0	1	0	0	1	0	0	0	1	0	0	1	0	1	0

Thermostat.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity Thermostat is port(
    CT : in std_logic_vector(3 downto 0);
    DT : in std_logic_vector(3 downto 0);
    OP : in std_logic_vector(2 downto 0);

    OTP : out std_logic_vector(6 downto 0)
);
end Thermostat;

architecture Logic of Thermostat is
    component Comp4 port(
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);
        GT : out std_logic;
        EQ : out std_logic;
        LE : out std_logic
    );
    end component;

    signal gt, eq, le : std_logic;
    signal tmp : std_logic_vector(2 downto 0);
    signal all_closed : std_logic;
    signal ctrl : std_logic_vector(3 downto 0);
    signal doors : std_logic_vector(2 downto 0);


begin
    comp4inst : Comp4 port map(CT, DT, gt, eq, le);
    -- Comparing current temp with desired temp
    tmp <= gt & eq & le;
    doors <= not(OP(2)) & not(OP(1)) & not(OP(0));
    all_closed <= OP(2) and OP(1) and OP(0);
    -- Since PBs are active-low, we don't need to NAND it
    with tmp&all_closed select
        ctrl <=
            --LEDS[7..0]
            "1001" when tmp : gt&eq&le&ALL_CLOSED
            "1100" when "0011", -- Furnace ON
            "0010" when "1001", -- A/C ON
            "0010" when "0101",
            "0010" when "0100",
            "0000" when others;

    OTP <= doors & ctrl;
end architecture Logic;
```


The Thermostat logic first compares desired and current temperature (each a 4 bit vector) using the 4 bit comparator declared earlier. We also inspect if all the windows/door are closed, to do so is fairly trivial, consider that the PBs are active-low, by applying AND to all 3 PB inputs, if such returns True, then we know all doors/windows are closed. For

implementing the logic of Thermostat, we used a straightforward case by case approach with our select statements.

Wave Simulation for 4-Bits Comparator

 

RTL Overview of LogicStep_3.vhd

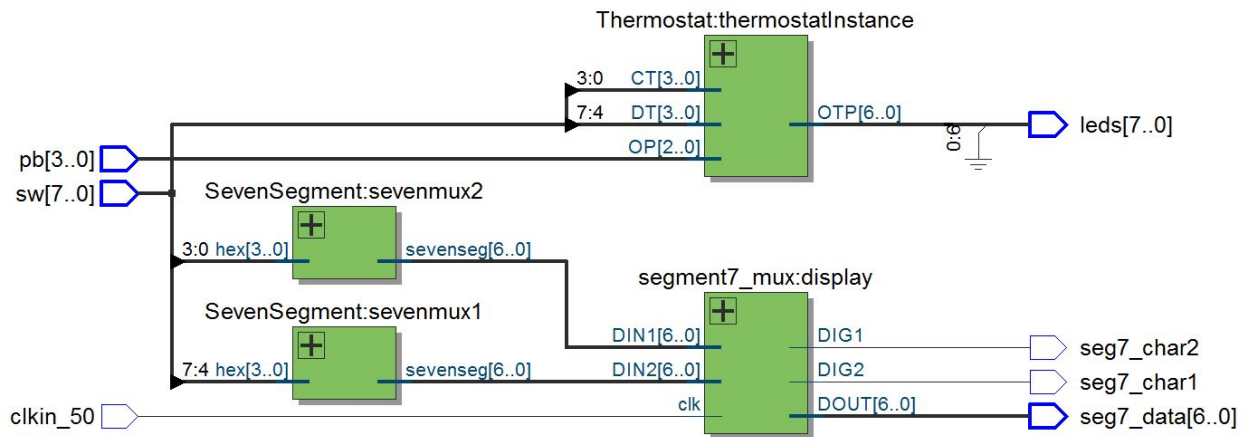

Number of Logical Elements Used: 47 /8064

Flow Status	Successful - Thu Mar 08 14:44:57 2018
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Standard Edition
Revision Name	LogicalStep_Lab3_top
Top-level Entity Name	LogicalStep_Lab3_top
Family	MAX 10
Device	10M08SAE144C8G
Timing Models	Final
Total logic elements	47 / 8,064 (< 1 %)
Total combinational functions	47 / 8,064 (< 1 %)
Dedicated logic registers	11 / 8,064 (< 1 %)
Total registers	11
Total pins	30 / 101 (30 %)
Total virtual pins	0
Total memory bits	0 / 387,072 (0 %)
Embedded Multiplier 9-bit elements	0 / 48 (0 %)
Total PLLs	0 / 1 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 1 (0 %)