 



ECE 124 digital circuits and systems

Assignment #10

Q1: Consider the asynchronous circuit shown below. Derive the transition table and flow table for the circuit. Remember to circle stable states.



 
Q2: Consider the asynchronous circuit shown below. Derive a transition table and flow table for the circuit. Draw waveforms for signals c , z_1 and z_2 assuming that c is a square wave clock signal and that each gate has a propagation delay of Δ units of time.



Q3: An asynchronous sequential circuit with two inputs x_1 and x_2 and one output z is described by the following equations and output functions: $Y = x_1x_2' + (x_1 + x_2')y$ and $z = y$. Here, Y 's represent the excitation variables (next state variables) and y 's represent the secondary variables (current state variables).

Draw the logic diagram of the circuit. Derive the transition table and flow table for the circuit.

 - Q4: A control mechanism for a vending machine accepts nickels and dimes. It dispenses merchandise when 20 cents is deposited; it does not give change if more than 20 cents is deposited. Design a state diagram assuming that the control mechanism will be implemented via an asynchronous sequential circuit (the state diagram might have a large number of states). When deriving your state diagram, assume that the circuit operates in fundamental mode (only one input changes at a time).
- Q5: Assume that you are to design an asynchronous sequential circuit with the following specifications. The circuit has two inputs c and w . The input c is a series of pulses. The output z replicates the input c when $w = 1$, otherwise $z = 0$. The pulses on z must be full pulses. That is, if $c = 1$ when w changes from $0 \rightarrow 1$, then the circuit will not produce a partial pulse on z but will wait until the next pulse to generate $z = 1$. If $c = 1$ when w changes from $1 \rightarrow 0$, then a full pulse must be generated. The desired operation is illustrated below.



Derive a primitive flow table for this problem assuming fundamental mode operation. Perform state minimization to obtain a reduced flow table. Finally, perform state assignment and derive a circuit.

- Q6: Obtain a state diagram and a primitive flow table for an asynchronous sequential circuit with two inputs x_1 and x_2 , and two outputs z_1 and z_2 . The circuit must have the following behaviour:
- When $x_1x_2 = 00$, the output is $z_1z_2 = 00$;
 - When $x_1 = 1$ and x_2 changes from $0 \rightarrow 1$, the output is $z_1z_2 = 01$;
 - When $x_2 = 1$ and x_1 changes from $0 \rightarrow 1$, the output is $z_1z_2 = 10$;
 - Otherwise, then output does not change.
- Q7: Consider an asynchronous sequential circuit with two inputs x_1 and x_2 , and one output z . Initially, both inputs are equal to 0. When either x_1 or x_2 becomes 1, the output z becomes 1. When the other input becomes 1, the output z changes back to 0. The output z remains 0 until both inputs return to 0 and the process repeats itself.

Assume fundamental mode operation. Derive a state diagram and a primitive flow table. Perform state minimization to show that the state table can be reduced to the following flow table.

Current State	Next State				Output (z)			
	$x_1x_2 = 00$	01	11	10	$x_1x_2 = 00$	01	11	10
a	\boxed{a}	\boxed{a}	b	\boxed{a}	0	1	-	1
b	a	\boxed{b}	\boxed{b}	\boxed{b}	-	0	0	0

Q8: Find a hazard-free minimum cost SOP implementations for the following functions:

- (a) $f(a, b, c, d) = \sum(0, 4, 11, 13, 15) + D(2, 3, 5, 10)$.
 (b) $f(a, b, c, d, e) = \sum(0, 4, 5, 24, 25, 29) + D(8, 13, 16, 21)$.

Q9: Find a hazard-free minimum cost POS implementations for the following functions:

- (a) $f(a, b, c, d) = \Pi(0, 2, 3, 7, 10) + D(5, 13, 15)$.
 (b) $f(a, b, c, d, e) = \Pi(2, 6, 7, 25, 28, 29) + D(0, 8, 9, 10, 11, 21, 24, 26, 27, 30)$.

Q10: Perform state minimization to reduce the following flow table to one with fewer states which exhibits the same functional behaviour.

Current State	Next State				Output z
	$x_1x_2 = 00$	01	11	10	
a	\boxed{a}	b	c	-	0
b	k	\boxed{b}	-	h	0
c	f	-	\boxed{c}	m	0
d	\boxed{d}	e	j	-	1
e	a	\boxed{e}	-	m	0
f	\boxed{f}	l	j	-	0
g	d	\boxed{g}	-	h	0
h	-	g	j	\boxed{h}	1
j	f	-	\boxed{j}	h	0
k	\boxed{k}	l	c	-	1
l	a	\boxed{l}	-	h	0
m	-	g	c	\boxed{m}	1

Q11: Consider the following flow table.

Current State	Next State				Output (z)			
	$x_1x_2 = 00$	01	11	10	$x_1x_2 = 00$	01	11	10
a	\boxed{a}	b	d	\boxed{a}	0	-	1	1
b	c	\boxed{b}	\boxed{b}	d	0	1	0	0
c	\boxed{c}	\boxed{c}	b	a	0	1	0	1
d	a	c	\boxed{d}	\boxed{d}	-	-	1	0


Find a suitable race-free state assignment which

- (a) Uses as few states as possible.

- (b) Uses the method of state duplication.
- (c) Uses the method of one-hot encoding.

Q12: Consider an asynchronous sequential circuit defined by the equations $Y = x_1x_2 + (x_1 + x_2)y$ and $z = y$. Implement this circuit using a NOR SR latch. Implement this circuit using a NAND $S'R'$ latch.

 Q13: Consider the circuit shown below which consists of two $S'R'$ latches.



Write down equations for the latch inputs S_1 , R_1 , S_2 and R_2 . Derive equations for the latch outputs Y_1 and Y_2 . Derive a transition table for the circuit.