 


Latches

- ▶ One type of *storage element* — exhibits the concept of memory.

SR latch


- ▶ We want a circuit in which we can force one output to 1, force the output to 0 and “hold” the output. Further, the circuit will have 2 outputs which are always *complements* of each other.
- ▶ The SR latch:



- ▶ There are 3 different cases to consider to see if this circuit does what we want and to figure out how it does it.

SR latch

 - ▶ Case I: Set $S = 1$ and $R = 0$. Then, change S to $1 \rightarrow 0$.
- ▶ The SR latch:




- ▶ Behaviour: By considering how a **NOR** gate works, setting $S = 1$ causes the bottom **NOR** to produce $\overline{Q} = 0$. The top **NOR** gate has inputs 00 and therefore produces $Q = 1$. We will call this the *set* state.
- ▶ Next, S is changed to 0. The bottom **NOR** gate now has inputs 10 which means that $\overline{Q} = 0$ still. The top **NOR** gate remains unchanged and $Q = 1$. We will call this the *memory or hold* state.
- ▶ Summary:

$$\begin{array}{ccccccc} S = 1 & R = 0 & \rightarrow & Q = 1 & \overline{Q} = 0 & \leftarrow & \text{set} \\ & & \downarrow & & & & \\ S = 0 & R = 0 & \rightarrow & Q = 1 & \overline{Q} = 0 & \leftarrow & \text{hold} \end{array}$$

SR latch

 - ▶ Case II: Set $S = 0$ and $R = 1$. Then, change R to $1 \rightarrow 0$.
- ▶ The SR latch:




- ▶ Behaviour: By considering how a **NOR** gate works, setting $R = 1$ causes the top **NOR** to produce $Q = 0$. The bottom **NOR** gate has inputs 00 and therefore produces $\overline{Q} = 1$. We will call this the *reset* state.
- ▶ Next, R is changed to 0. The top **NOR** gate now has inputs 01 which means that $Q = 0$ still. The bottom **NOR** gate remains unchanged and $\overline{Q} = 1$. We will call this the *memory* or *hold* state.
- ▶ Summary:

$$\begin{array}{ccccccc} S = 0 & R = 1 & \rightarrow & Q = 0 & \overline{Q} = 1 & \leftarrow & \text{reset} \\ & & \downarrow & & & & \\ S = 0 & R = 0 & \rightarrow & Q = 0 & \overline{Q} = 1 & \leftarrow & \text{hold} \end{array}$$

SR latch

 - ▶ Case III: Set $S = 1$ and $R = 1$.
- ▶ The SR latch:



- ▶ With both $S = 1$ and $R = 1$ we see that both $Q = 0$ and $\bar{Q} = 0$ which should be troubling — the outputs are no longer complements of each other.
- ▶ Now assume that both S and R change to 0. Different things could happen...
- ▶ We will call the situation with $S = 1$ and $R = 1$ the *restricted* or *undesireable* state.

SR latch


- ▶ Case III: Change $S = 1 \rightarrow 0$ and $R = 1 \rightarrow 0$.
- ▶ Both **NOR** gates have inputs 00 which means their outputs need to change... But we can assume things change at different times...
- ▶ Assume that Q changes first from $Q = 0 \rightarrow 1$.
 - ▶ This means the bottom **NOR** gate will inputs 10 and so $\overline{Q} = 0$.
 - ▶ In this case, the different circuit values are $S = 0$, $R = 0$ and $Q = 1$ and $\overline{Q} = 0$.
- ▶ Assume that \overline{Q} changes first from $\overline{Q} = 0 \rightarrow 1$.
 - ▶ This means the top **NOR** gate will inputs 01 and so $Q = 0$.
 - ▶ In this case, the different circuit values are $S = 0$, $R = 0$ and $Q = 0$ and $\overline{Q} = 1$.
- ▶ Assume that both Q and \overline{Q} changes at the same time from $Q = 0 \rightarrow 1$ and $\overline{Q} = 0 \rightarrow 1$.
 - ▶ But this means that both **NOR** gates will now have inputs 01 so there outputs should change back to $Q = 0$ and $\overline{Q} = 0$.
 - ▶ This situation could cause *oscillations*.
- ▶ The bottom line is that $S = 1$ and $R = 1$ is an input combination that should be avoided.

SR latch

- ▶ We can avoid $S = 1$ and $R = 1$ by adding additional logic at the inputs such that we never get this input.
- ▶ If we add logic such that $S = 1$ and $R = 1$ causes the outputs to become $Q = 1$ and $\overline{Q} = 0$, we have a *set dominated latch*.
- ▶ If we add logic such that $S = 1$ and $R = 1$ causes the outputs to become $Q = 0$ and $\overline{Q} = 1$, we have a *reset dominated latch*.
- ▶ We could do something else like have $S = 1$ and $R = 1$ cause the latch to *flip* or *toggle* its outputs. In this case we will get a *JK latch*.

SR latch

- Summary:
- The SR latch:

 

- Tabular description:


S	R	Q	\bar{Q}	Action
1	0	1	0	set
0	1	0	1	reset
0	0	1	0	memory or hold after $S = 1, R = 0$
0	0	0	1	memory or hold after $S = 0, R = 1$
1	1	?	?	restricted

- As an equation ($Q(t+1)$ is the "next value of Q and $Q(t)$ is the current value of Q):

$$Q(t+1) = Q(t)\bar{R} + S\bar{R}$$

$\overline{S} \overline{R}$ latch

 
- ▶ Can build a similar circuit using **NAND** gates, but the operation is a little bit different.
- ▶ The $\overline{S} \overline{R}$ latch:



- ▶ We could do analysis similar to the SR latch and conclude there is a *set*, *reset*, *hold* and *restricted* case.

$\overline{S} \overline{R}$ latch

 - ▶ Summary:
- ▶ The $\overline{S} \overline{R}$ latch:



- ▶ Tabular description:

S	R	Q	\overline{Q}	Action
1	0	0	1	reset
0	1	1	0	set
1	1	0	1	memory or hold after $S = 1, R = 0$
1	1	1	0	memory or hold after $S = 0, R = 1$
0	0	?	?	restricted


- ▶ As an equation ($Q(t+1)$ is the “next value of Q and $Q(t)$ is the current value of Q):

$$Q(t+1) = Q(t)R + \overline{S}R$$

- ▶ Note the bubbles on the S and R inputs; this tends to be described as “active low” inputs.

Gated D latch


- ▶ The gated D latch:

 

- ▶ The D input is called the *data* input and the G input is called the *gate* input.

Gated D latch


- ▶ Case I:

 

- ▶ If $G = 1$ and $D = 1$, then the output is set.

Gated D latch


► Case II:

 

- If $G = 1$ and $D = 0$, then the output is *reset*.

Gated D latch

► Case III:

 


- If $G = 0$ the value of D is not relevant; the outputs remain at their previous value and *hold*.

Gated D latch

- Behaviour of the D latch:

D	G	Q	\overline{Q}	Action
1	1	1	0	\leftarrow set
0	1	0	1	\leftarrow reset
0/1	0	<i>previous value</i>		\leftarrow hold

 - Note that we don't need to worry about any “restricted” cases like with the SR latch or the $\overline{S} \overline{R}$ latch.
- Symbol:



- As an equation ($Q(t+1)$ is the “next value of Q and $Q(t)$ is the current value of Q):

$$Q(t+1) = DG + Q(t)\overline{G}$$

Latch summary

- ▶ There are other configurations and types of latches, but these ones are enough for our purposes.
- ▶ We won't do too much with latches depending on time, but they are useful for a number of things...
- ▶ One last comment... Latches are an example of a *level sensitive* storage element — the outputs are *set*, *reset* or *hold* depending on the logic levels/values of the inputs.