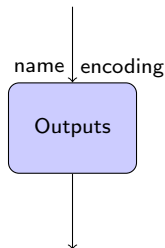


# Algorithmic state machines

- ▶ An algorithmic state machine (ASM) is simply an alternative to the state diagram — it looks a bit more like a flow chart.
- ▶ Consists of three types of boxes.
  - ▶ State boxes;
  - ▶ Decision boxes;
  - ▶ Conditional output boxes.

# Algorithmic state machines — state boxes


- ▶ The state box is rectangular and is equivalent to the state bubble in a state diagram.
- ▶ The box has the state name or its binary encoding listed above the box.
- ▶ Any outputs that are 1 and that depend only on the state are labeled inside of the box.
- ▶ The state box has one entry point and one exit point.
- ▶ Example...



- ▶ **Note:** Outputs are only shown in the ASM when they are 1.

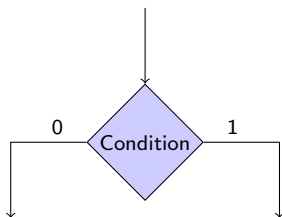
# Algorithmic state machines — decision boxes

- ▶ The decision box is a diamond shaped box with one entry point and two exit points.
- ▶ The inside of the box is labeled with an arbitrary logic expression which evaluates to 0 or 1; the evaluation will cause one of the exit points to be chosen.
- ▶ Example...


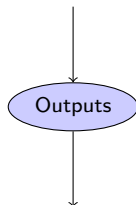
# Algorithmic state machines — conditional output boxes

- ▶ The conditional output box has one entry and one exit. It specifies an output that occurs when a transition takes place.
- ▶ These boxes are required if we have a circuit with Mealy outputs.
- ▶ Example...




**Note:** Outputs are only shown in the ASM when they are 1.

# Algorithmic state machines

- ▶ Designing a circuit given an ASM is exactly the same as if one was given a state diagram.
- ▶ You can identify the number of states by the number of state boxes.
- ▶ You can determine the next state and transitions based on the decision boxes.
- ▶ You can determine the circuit outputs based on the decision boxes and conditional output boxes.
- ▶ This will lead to a completed state table and the rest of the design is the same as before (do state assignment, find logic equations, etc.)

# Algorithmic state machines

## ► Example...

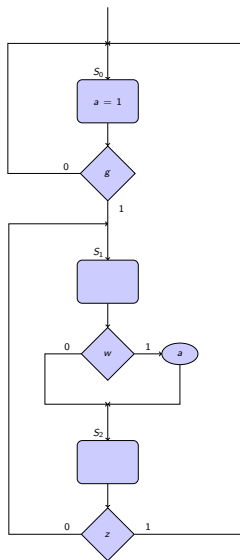

# Algorithmic state machines


- ▶ Example clearly has 3 states  $S_0$ ,  $S_1$  and  $S_2$  since there are 3 state boxes.
- ▶ Example clearly has 3 inputs  $g$ ,  $w$  and  $z$  since there are 3 decision boxes and these variables are labeled inside the decision boxes.
- ▶ Example clearly has 1 output  $a$  which is labeled inside of the state box  $S_0$  and in a conditional output box. Clearly  $a$  is 1 when in state  $S_0$  or in state  $S_1$  and  $w = 1$ , otherwise 0.
- ▶ Symbolic state table (written in a slightly different form due to the number of don't care situations in the decision boxes and the large number of inputs):

| Current state | Input |     |     | Next state | Output<br>$a$ |
|---------------|-------|-----|-----|------------|---------------|
|               | $g$   | $w$ | $z$ |            |               |
| $S_0$         | 0     | X   | X   | $S_0$      | 1             |
| $S_0$         | 1     | X   | X   | $S_1$      | 1             |
| $S_1$         | X     | 0   | X   | $S_2$      | 0             |
| $S_1$         | X     | 1   | X   | $S_2$      | 1             |
| $S_2$         | X     | X   | 0   | $S_1$      | 0             |
| $S_2$         | X     | X   | 1   | $S_0$      | 0             |

- ▶ From here, we perform state assignment, pick a flip flop type, derive next state functions and output functions, etc.
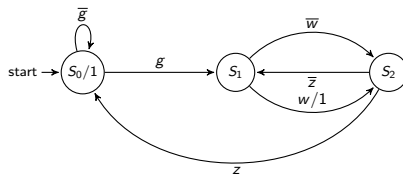
# Algorithmic state machines

- ▶ You should be able to convert this ASM into a state diagram (and do the reverse procedure if required).



- ▶ Note this diagram is sort of a hybrid — sometimes output is shown inside the state bubble and sometimes on the edges.




# Algorithmic state machines — one hot encoding

- ▶ It is particularly easy to implement an ASM using one hot encoding because every box in the ASM corresponds to a circuit element.
- ▶ We might need some additional **OR** gates here and there.


# Algorithmic state machines — one hot encoding

## ► State box...

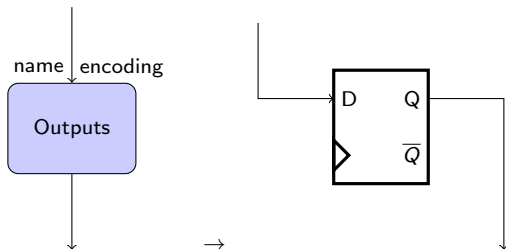


# Algorithmic state machines — one hot encoding

► Decision box...

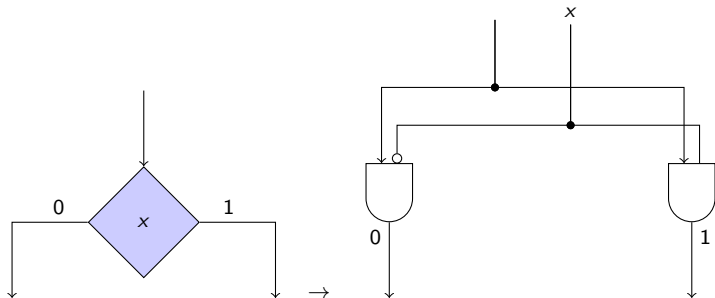

# Algorithmic state machines — one hot encoding

- ▶ Conditional output box...

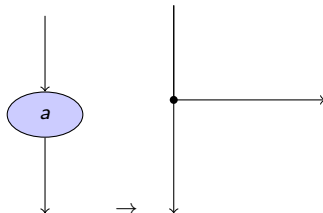

We simply “tap off” from the wire passing through the conditional output box.


- ▶ Joining...



Joining arrows become and **OR** gate.
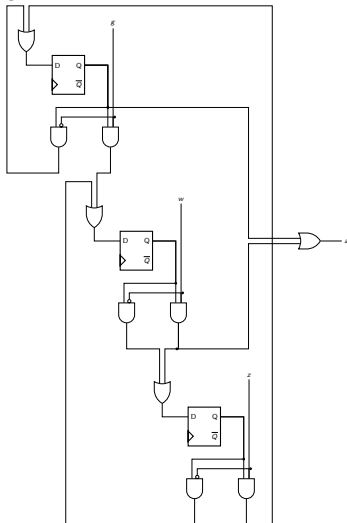
# Algorithmic state machines — one hot encoding

- The circuit we would get from our ASM...



- Of course, you can look at the ASM and write down equations for the *DFF* inputs and circuit outputs too.