

# ECE 124 digital circuits and systems

## Assignment #6

Q1: Show how a JK flip-flop can be implemented with a T flip-flop and other logic gates.

**Solution:**


Start with the table describing how a *JKFF* works. Then, find the values for a *TFF* necessary to get the desired changes — the values for *T* are found by comparing *Q(t)* and *Q(t + 1)* for the *JKFF*.

<i>J</i>	<i>K</i>	<i>Q(t)</i>	<i>Q(t + 1)</i>	<i>T</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

Next, write down the equation for *T*:

$$\begin{aligned}
 T &= \bar{J}KQ(t) + J\bar{K}\bar{Q}(t) + JK\bar{Q}(t) + JKQ(t) \\
 &= +J\bar{Q}(t) + KQ(t)
 \end{aligned}$$


The circuit...

 


Q2: Assume that you have a 100-MHz clock signal. Derive a circuit using D flip-flops to generate a 50-MHz and 25-MHz clock signal. Draw a timing diagram for all three clock signals.

**Solution:**

Circuit...

 

The timing diagram...

 

Q3: Shown below is a gated  $SR$  latch and a table explaining its operation.


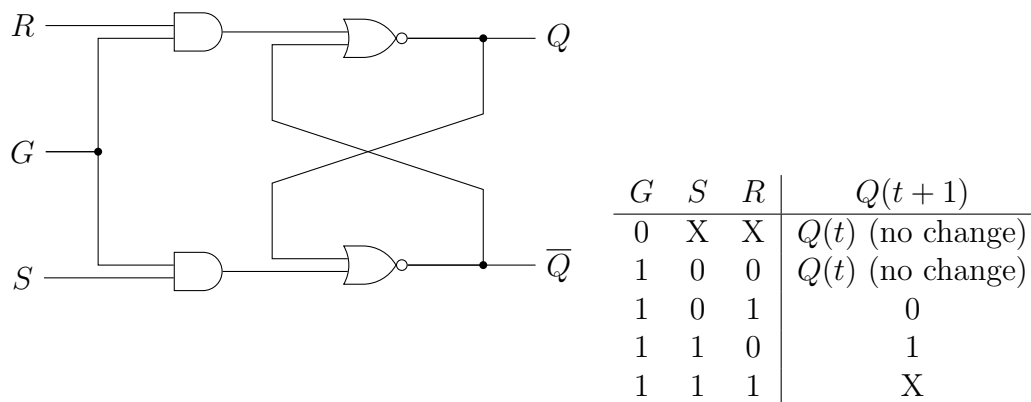


Figure 1: Gated  $SR$  latch for Problem 3.

This latch has undefined behaviour when  $S = 1$  and  $R = 1$  and  $G$  changes from 1 to 0. This problem can be solved by making a *set dominated gated  $SR$  latch* in which  $S = 1$  and  $R = 1$  causes the latch to be set to 1. Design a set dominated gated  $SR$  latch and draw its circuit.

 
**Solution:** Mark the inputs to the regular  $SR$  latch as  $R^*$  and  $S^*$ .



The problem happens when  $G = 1$ ,  $R = 1$  and  $S = 1$  because this causes  $R^* = 1$  and  $S^* = 1$ . We would like  $R^* = 0$  and  $S^* = 1$  when  $G = 1$ ,  $R = 1$  and  $S = 1$ . Shown below is what we have as well as what we would want.

$G$	$S$	$R$	$S^*$	$R^*$		$G$	$S$	$R$	$S^*$	$R^*$	
0	X	X	0	0		0	X	X	0	0	
1	0	0	0	0		1	0	0	0	0	
1	1	0	1	0		1	1	0	1	0	
1	0	1	0	1		1	0	1	0	1	
1	1	1	1	1	← bad	1	1	1	1	0	← set dominated

 Therefore, we only need to change the equation for  $R^*$  to  $R^* = GR\bar{S}$ . In other words, add an inverter as shown:



Q4: An  $SR$  flip flop is a flip-flop that has set and reset inputs like a gated  $SR$  latch. Show how to construct an  $SR$  flip-flop using a  $D$  flip-flop and other logic gates.


**Solution:**

Start with the table for the gated  $SR$  latch. Then, figure out what the  $DFF$  input needs to be in each case to obtain the desired behaviour (Note that the gate  $G$  becomes the clock input).


$S$	$R$	$Q(t)$	$Q(t+1)$	$D$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	X	X
1	1	1	X	X

Since the inputs  $S = 1$  and  $R = 1$  are undefined, they become don't care conditions.

 We can use a Karnaugh map to find the optimized expression for  $D$  is  $D = S + \overline{R}Q(t)$ . We get the following circuit.



 
Q5: Consider the timing diagram below which shows a clock signal and a data input signal connected to the inputs of a gated D-latch, a positive edge triggered DFF and a negative edge triggered DFF. Draw the outputs  $Q_a$ ,  $Q_b$  and  $Q_c$  for each of the elements.




**Solution:**

1. The gated  $D$  latch output holds when  $G = 0$  and outputs  $D$  when  $G = 1$ .
2. Positive edge triggered  $DFF$  samples  $D$  at the rising edge of the clock and keeps that value for one clock period until the next rising edge.
3. Negative edge triggered  $DFF$  samples  $D$  at the falling edge of the clock and keeps that value for one clock period until the next falling edge.


Therefore...

 

 
Q6: Consider the  $SR$  latch shown below and the accompanying timing diagram — this problem is intended to illustrate the improper operation of the latch if both inputs of the latch are 1 and then changed to 0 at the same time.



 Complete the following timing chart. Assume that  $P = 1$  and  $Q = 0$  initially. Assume that each NOR gate has a delay of  $10ns$ . Note that when  $t = 100ns$ ,  $S$  and  $R$  are both changed to 0. Then,  $10ns$  later, both  $P$  and  $Q$  will change to 1. Because the 1's are fed back to the gate inputs, what will happen after another  $10ns$ ?




**Solution:**

 

1. Initially both  $S = 0$  and  $R = 0$  which means hold.
2. At  $50ns$ , both  $S$  and  $R$  change to 1 which is the undefined state. Both **NOR** gates will output 0, but it takes  $10ns$  for  $P$  to change to 0.
3. As long as  $S$  and  $R$  are 1, both outputs are 0 and remain 0.
4. At  $100ns$ ,  $S$  and  $R$  change to 0. Both **NOR** gates change and  $P$  and  $Q$  change to 1 after  $10ns$ .
5. As long as  $S$  and  $R$  are 0, the  $P$  and  $Q$  will propagate back to the **NOR** gate inputs and cause the output to continually flip back and forth.
6. Once  $P = 1$  at  $140ns$ , the latch enters the set state and  $P = 1$  and  $Q = 0$  after  $10ns$ .

 Q7: Complete the following timing diagram for a  $JK$  flip-flop.



**Solution:**

We just need to recall how a  $JKFF$  works.  $JK = 00$  means hold,  $JK = 11$  means toggle,  $JK = 10$  means set and  $JK = 01$  means reset.

