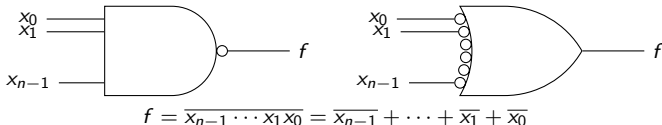


Circuits implemented with only **NAND** and/or **NOR**


- ▶ We can implement any circuit with **AND**, **OR**, and **NOT** gates, but we can implement any circuit using *only* **NAND** or **NOR** (or a combination of the two types).
- ▶ We might do this for certain considerations — e.g., due to technology considerations where **NAND** and **NOR** gates are cheaper to implement.
- ▶ The ability to use only **NAND** or **NOR** follows from the observation that we can make **AND**, **OR**, and **NOT** gates with only **NAND** or **NOR** gates.

Circuits implemented with only **NAND** and/or **NOR**

- Useful to note that an **NAND** gate performs the same operation as an **OR** gate that has inverted inputs:



- Useful to note that an **NOR** gate performs the same operation as an **AND** gate that has inverted inputs:

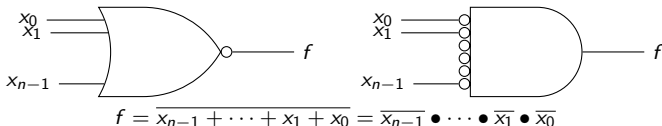

Converting 2-level SOP to **NAND** only

- ▶ Given a SOP obtaining a NAND only implementation is trivial — apply a double inversion and use the DeMorgan theorem being careful of where we leave the inversions in the final expression.
- ▶ Example...

$$\begin{aligned} f &= x_1!x_2 + !x_1x_2 + x_3 \\ &= !(!f) \\ &= !(!(x_1!x_2 + !x_1x_2 + x_3)) \\ &= !(!(x_1!x_2)!(!x_1x_2)!(x_3)) \\ &\quad \text{NAND} \quad \text{NAND} \quad \text{INV} \\ &= \underbrace{!(!(x_1!x_2)!(!x_1x_2)!(x_3))}_{\text{NAND}} \end{aligned}$$

Converting 2-level POS to **NOR** only

- ▶ Given a POS obtaining a **NOR** only implementation is trivial — apply a double inversion and use the DeMorgan theorem being careful of where we leave the inversions in the final expression.
- ▶ Example...


$$\begin{aligned} f &= (x1 + x2)(x3 + x4)(x5) \\ &= \neg(\neg f) \\ &= \neg(\neg((x1 + x2)(x3 + x4)(x5))) \\ &= \neg(\neg(x1 + x2) + \neg(x3 + x4) + \neg(x5)) \\ &= \underbrace{\neg(\underbrace{\neg(x1 + x2)}_{NOR} + \underbrace{\neg(x3 + x4)}_{NOR} + \underbrace{\neg(x5)}_{INV})}_{NOR} \end{aligned}$$

Multi-level circuit conversions

- ▶ For circuits which are not SOP or POS we can still do the conversion (note that this also works for SOP or POS)...
- ▶ Insert “double inversions” where necessary to convert gates appropriately.
- ▶ We might end up with some left-over inverters, but that’s okay.


Multi-level circuit conversions — conversion to **NAND**

- ▶ To convert to **NAND**: 1. Insert double inversions prior to each **OR**; 2. Insert double inversions after every **AND** gate; 3. Convert gates and cancel out any remaining double inversions.
- ▶ Note that there might be some left-over inverters. Note that the use of double inversion ensures that the circuit doesn't change its operation.
- ▶ Example: Convert the following to **NAND** only gates.

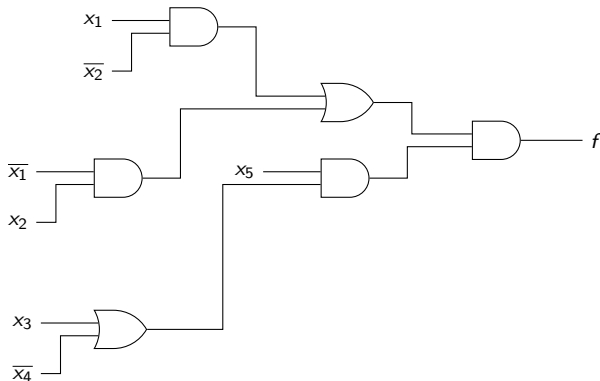


Multi-level circuit conversions — conversion to **NAND**

- ▶ To convert to **NAND**: 1. Insert double inversions prior to each **OR**; 2. Insert double inversions after every **AND** gate; 3. Convert gates and cancel out any remaining double inversions.
- ▶ Note that there might be some left-over inverters. Note that the use of double inversion ensures that the circuit doesn't change its operation.
- ▶ Example: Convert the following to **NAND** only gates.

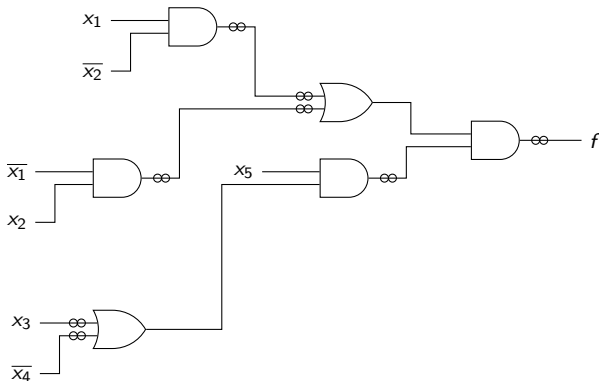


Multi-level circuit conversions — conversion to **NAND**

- ▶ To convert to **NAND**: 1. Insert double inversions prior to each **OR**; 2. Insert double inversions after every **AND** gate; 3. Convert gates and cancel out any remaining double inversions.
- ▶ Note that there might be some left-over inverters. Note that the use of double inversion ensures that the circuit doesn't change its operation.
- ▶ Example: Convert the following to **NAND** only gates.

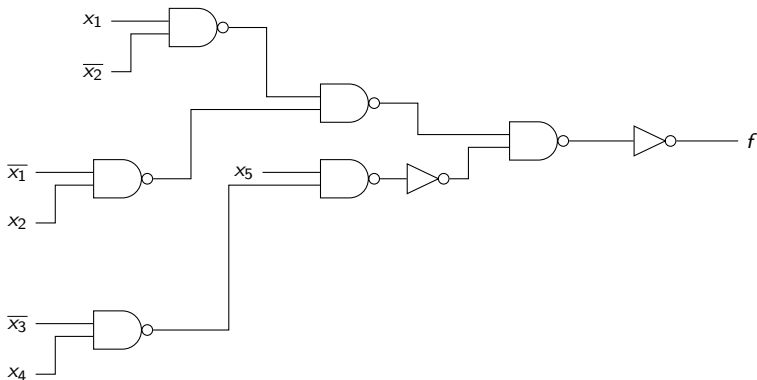

Multi-level circuit conversions — conversion to **NOR**

- ▶ To convert to **NOR**: 1. Insert double inversions prior to each **AND**; 2. Insert double inversions after every **OR** gate; 3. Convert gates and cancel out any remaining double inversions.
- ▶ Note that there might be some left-over inverters. Note that the use of double inversion ensures that the circuit doesn't change its operation.
- ▶ Example: Convert the following to **NOR** only gates.

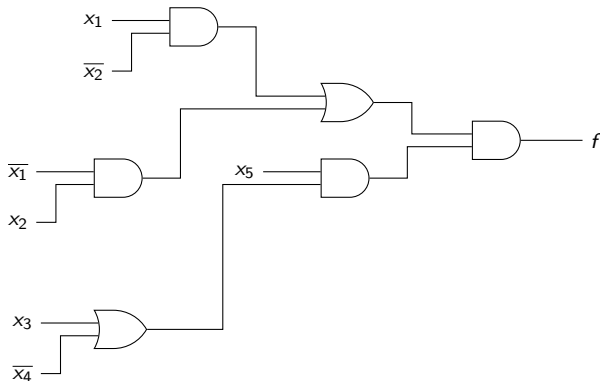

Multi-level circuit conversions — conversion to **NOR**

- ▶ To convert to **NOR**: 1. Insert double inversions prior to each **AND**; 2. Insert double inversions after every **OR** gate; 3. Convert gates and cancel out any remaining double inversions.
- ▶ Note that there might be some left-over inverters. Note that the use of double inversion ensures that the circuit doesn't change its operation.
- ▶ Example: Convert the following to **NOR** only gates.

