

ECE 124 digital circuits and systems

Assignment #2

- Q1: Design the simplest circuit that has 3 inputs, x_1 , x_2 and x_3 , which produces an output of 1 whenever exactly one or two of the inputs have the value of 1; otherwise, the output is 0.
- Q2: Consider a circuit with one output f and four inputs a_1 , a_0 , b_1 and b_0 . Let $A = a_1a_0$ be a binary representation of a number where the four possible values of A (00, 01, 10, and 11) represent the four unsigned integer values 0, 1, 2 and 3, respectively. Similarly, let $B = b_1b_0$ represent another number with the same four values. Assume that f should be 1 if the numbers represented by A and B are equal, otherwise f should be 0.
- (a) Provide the truth table for f ;
 - (b) Determine the simplest product-of-sums expression for f .
- Q3: Consider a circuit with one output f and four inputs a_1 , a_0 , b_1 and b_0 . Let $A = a_1a_0$ be a binary representation of a number where the four possible values of A (00, 01, 10, and 11) represent the four unsigned integer values 0, 1, 2 and 3, respectively. Similarly, let $B = b_1b_0$ represent another number with the same four values. Assume that f should be 1 if $A \geq B$, otherwise f should be 0.
- (a) Provide the truth table for f ;
 - (b) Determine the simplest sum-of-products expression for f .
- Q4: Consider the following sum-of-products expression $f = x'_1x'_2x_3 + x'_1x_2x'_3 + x_1x'_2x'_3 + x_1x_2x_3$. Implement f as a 2-level circuit using only NAND gates.
- Q5: Consider the following product-of-sums expression $f = (x_1 + x'_2 + x'_3)(x'_1 + x_2 + x'_3)(x'_1 + x'_2 + x_3)(x_1 + x_2 + x_3)$. Implement f as a 2-level circuit using only NOR gates.
- Q6: Consider the logic function $f = (((x_1x'_2) + (x'_1x_2))x_3) + (((x_1x'_2) + (x'_1x_2))'x_4)$ which is shown below (note that inverters are shown explicitly) in Figure 1.
- (a) Implement/convert this circuit to one that uses only NAND gates and NOT gates.
 - (b) Implement/convert this circuit to one that uses only NOR gates and NOT gates.
- Q7: Consider the logic function $f = (AB' + CD')E + BC(A + B)$.
- (a) Draw this multi-level circuit using AND, OR and NOT gates.
 - (b) Convert and draw a multi-level circuit implementation that uses only NAND gates and NOT gates.

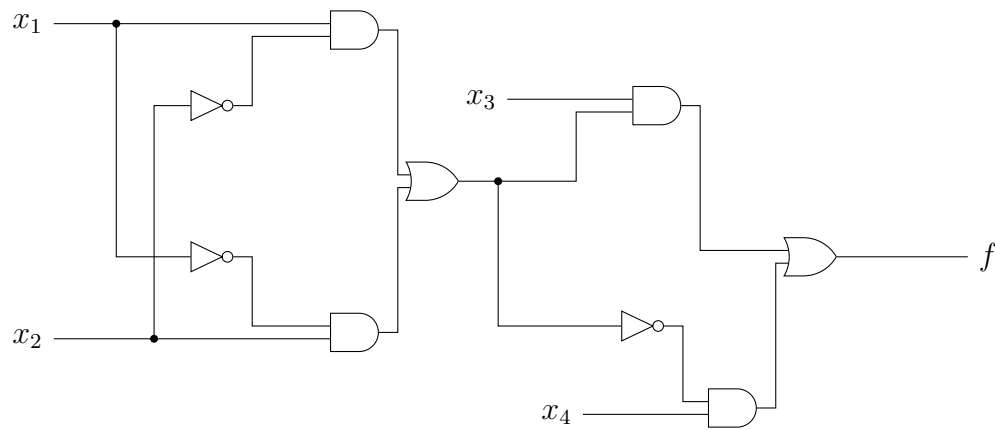


Figure 1: Circuit for Q6.

Q8: Consider the logic function $f = w(x + y + z) + xyz$.

- (a) Draw this multi-level circuit using AND, OR and NOT gates.
- (b) Convert and draw a multi-level circuit implementation that uses only NOR gates and NOT gates.