

# ECE 124 digital circuits and systems

## Assignment #6

- Q1: Show how a JK flip-flop can be implemented with a T flip-flop and other logic gates.
- Q2: Assume that you have a 100-MHz clock signal. Derive a circuit using D flip-flops to generate a 50-MHz and 25-MHz clock signal. Draw a timing diagram for all three clock signals.
- Q3: Shown below is a gated *SR* latch and a table explaining its operation.


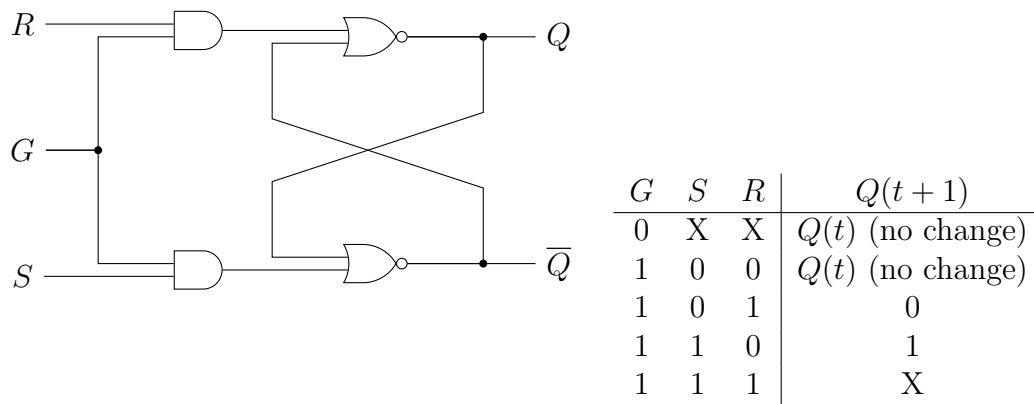


Figure 1: Gated SR latch for Problem 3.


This latch has undefined behaviour when  $S = 1$  and  $R = 1$  and  $G$  changes from 1 to 0. This problem can be solved by making a *set dominated gated SR latch* in which  $S = 1$  and  $R = 1$  causes the latch to be set to 1. Design a set dominated gated *SR* latch and draw its circuit.

- Q4: An *SR* flip flop is a flip-flop that has set and reset inputs like a gated *SR* latch. Show how to construct an *SR* flip-flop using a *D* flip-flop and other logic gates.

 
Q5: Consider the timing diagram below which shows a clock signal and a data input signal connected to the inputs of a gated D-latch, a positive edge triggered DFF and a negative edge triggered DFF. Draw the outputs  $Q_a$ ,  $Q_b$  and  $Q_c$  for each of the elements.



 Q6: Consider the  $SR$  latch shown below and the accompanying timing diagram — this problem is intended to illustrate the improper operation of the latch if both inputs of the latch are 1 and then changed to 0 at the same time.



 Complete the following timing chart. Assume that  $P = 1$  and  $Q = 0$  initially. Assume that each NOR gate has a delay of  $10ns$ . Note that when  $t = 100ns$ ,  $S$  and  $R$  are both changed to 0. Then,  $10ns$  later, both  $P$  and  $Q$  will change to 1. Because the 1's are fed back to the gate inputs, what will happen after another  $10ns$ ?



Q7: Complete the following timing diagram for a  $JK$  flip-flop.

